



Politecnico di Torino

Microelectronic Systems

DLX Microprocessor: Design & Development

Final Project Report

Master degree in Electronics Engineering

Master degree in Computer Engineering

Referents: Prof. Mariagrazia Graziano, Giovanna Turvani

Authors: Group 52

name1, name2

October 17, 2023

Contents

1	Introduction	1
1.1	Specifications	1
2	Functional schema	2
2.1	Datapath	2
2.2	Functional blocks	3
2.2.1	Control unit	3
2.2.2	Register file	3
2.2.3	ALU	3
2.2.4	Hazard detection unit	4
2.2.5	Forwarding unit	4

CHAPTER 1

Introduction

1.1 Specifications

CHAPTER 2

Functional schema

2.1 Datapath

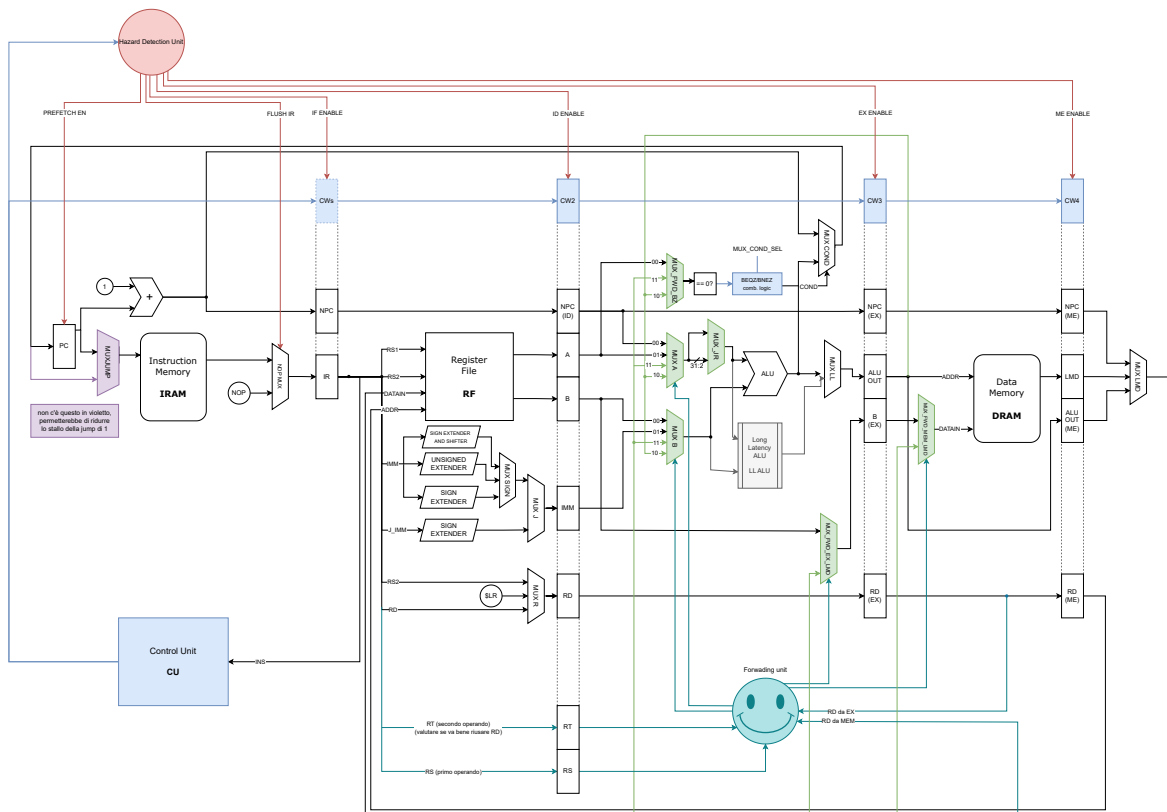


Figure 2.1: sus

2.2 Functional blocks

2.2.1 Control unit

2.2.2 Register file

2.2.3 ALU

The ALU of the DLX operates on two inputs: *DATA1* and *DATA2*. The function to be computed on the operands is selected by a third input *FUNC* that receives a code representing it and the result is sent to the output *OUTALU*. A list of currently implemented functions follows. The implementation of each operation is behavioural unless specified otherwise.

Addition

$$ALUOUT = DATA1 + DATA2$$

A P4 adder is present inside the ALU to perform additions. Further details on its implementation together with the VHDL description are included in lab 2's zip file.

Subtraction

$$ALUOUT = DATA1 - DATA2$$

The P4 adder is also used for subtractions, by means of negating one of the inputs and setting the carry-in input of the adder to 1.

Multiplication

$$ALUOUT = DATA1 \cdot DATA2$$

Multiplication is executed on the operands fully but the result is still word size: the most significant half of the computed value is discarded.

AND

$$ALUOUT = DATA1 \wedge DATA2$$

OR

$$ALUOUT = DATA1 \vee DATA2$$

XOR

$$ALUOUT = DATA1 \oplus DATA2$$

Logical Shift Left

$$ALUOUT = DATA1 \ll DATA2$$

Logical Shift Right

$$ALUOUT = DATA1 \gg DATA2$$

Set equal

if(*DATA1* == *DATA2*) *then* *ALUOUT* = 1 *else* 0

Set not equal

if($DATA1 \neq DATA2$) *then* $ALUOUT = 1$ *else* 0

Set greater than or Equal (signed and unsigned)

if($DATA1 \geq DATA2$) *then* $ALUOUT = 1$ *else* 0

Set greater than (signed and unsigned)

if($DATA1 > DATA2$) *then* $ALUOUT = 1$ *else* 0

Set less than or Equal (signed and unsigned)

if($DATA1 \leq DATA2$) *then* $ALUOUT = 1$ *else* 0

Set less than (signed and unsigned)

if($DATA1 < DATA2$) *then* $ALUOUT = 1$ *else* 0

2.2.4 Hazard detection unit**2.2.5 Forwarding unit**